

Circuit Notes Part 2

Series circuits

A series circuit has 1 pathway(s).

This means current must go through all

resistors. Since they are going through all

resistors there is high resistance. Since

there is high resistance there will be

low current intensity. If you add

another resistor to the circuit the resistance of

the circuit increases which will cause the

current intensity to decrease.

Therefore, current intensity and resistance have

an inverse relationship.

If you increase the power supply voltage, the

resistance will stay the same, but the




current intensity will decrease.

Resistors do not effect voltage

coming from the power supply and the voltage

from the power supply

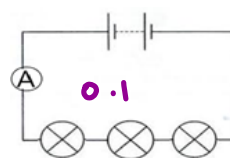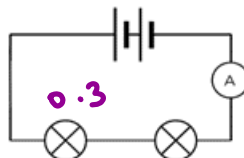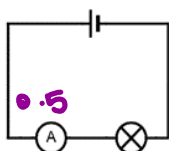does not affect resistors in the circuit.



Parallel circuit

A parallel circuit has multiple pathway(s).

This means current will be shared

amongst the resistors. Since current is not going through each resistor, the resistance of the circuit

is low. Since the resistance is

low, the current intensity of the circuit will be



high. Current intensity and

resistance still have an inverse

relationship. As you add light bulbs, the

brightness stays the same because

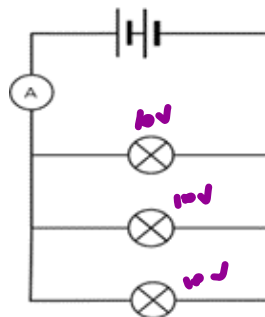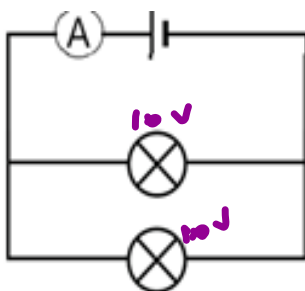each light bulb is getting the total voltage.



To summarize:

Series circuit = 1 pathway = high resistance = low current intensity

Parallel circuit = 2 pathways = low resistance = high current intensity

Power and Energy Formulas

What will occur to power and energy results if voltage from the power supply is kept constant and the same resistors are used in a series vs a parallel circuit?

The series circuit will have a lower power and energy then the parallel circuit because the current intensity value will be lower since there is a higher resistance.

Understanding values: using two 50 Ω resistors and PS set to 4 V.

	Resistance (Ω)	Current intensity (A)	Voltage (V)
Series	100	.04	4
Parallel	25	.16	4

$P = I \cdot V$		$E = I \cdot V \cdot t$	
Power series	Power parallel	Energy series	Energy parallel
$.4 \times 4 = 1.6 \text{ W}$	$.16 \times 4 = .64 \text{ W}$	$.4 \times 4 \times 1 = 1.6 \text{ J}$	$.16 \times 4 \times 1 = .64 \text{ J}$

Recap:

series = high resistance = low CI = low power and energy

parallel = low resistance = high CI = high power and energy

Past exam questions


1. Jeremy assembled an electrical circuit using a 6 V battery and a resistor. He measured a current intensity of 0.05 A in this circuit.
- a- What is the resistance of this circuit?

$$R = \frac{V}{I} = \frac{6}{0.05} = 120 \Omega$$

b- If the 6 V battery is replaced with a battery with a greater potential difference (voltage), and the same resistor is used, what will happen to the electric current intensity in this circuit?

- 1- The electric current intensity will increase
 2- The electric current intensity will decrease
 3- The electric current intensity will remain the same

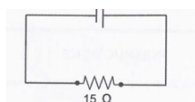2. The following circuit has a power source and a resistor.



Which of the following correctly describes a consequence of a change made to one of the components of this circuit?

- 1) The potential difference across the terminals of the resistor will increase if a 10 Ω resistor is used instead.
 2) The current intensity of the circuit will increase if a 10 Ω resistor is used instead.
 3) The resistance will remain the same even if the potential difference across the terminals of the source is increased.
 4) The current intensity of the circuit will remain the same even if the potential difference across the terminals of the power source is increased without changing the resistor.
 5) The current intensity of the circuit will increase if the potential difference across the terminals of the power source is increased without changing the resistor.

A) 2 and 3 C) 2, 3 and 5

B) 1 and 3 D) 1, 3 and 5

3. A student takes two 15 Ω resistors and places them in a series. He sets the power supply to 20 V and takes the current intensity measurement from the power source. He then uses the same resistors and places them in a parallel. If he keeps the voltage still at 20V, what should happen to the current intensity value when he measures it from the power source

A) The current intensity value will increase because there is more resistance in a parallel circuit.

B) The current intensity value will increase because there is less resistance in a parallel circuit.

C) The current intensity value will decrease because there is more resistance in a parallel circuit.

D) The current intensity value will decrease because there is less resistance in a parallel circuit.