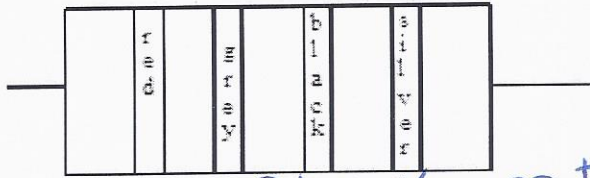


Circuit Worksheet 1


1. Using the international color code, determine the value of the resistances the two resistors 1 and 2.

Resistor 1







$$28 \times 10^3 \pm 10\% \text{ or } 28 \text{ k}\Omega \pm 10\%$$

Resistor 2

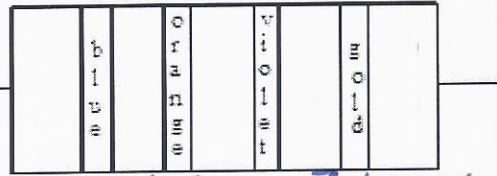


$$63 \times 10^1 \pm 5\%$$

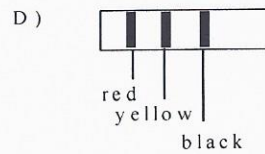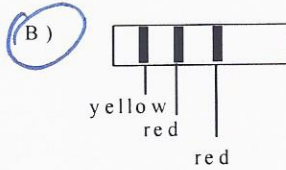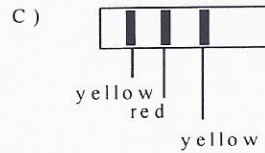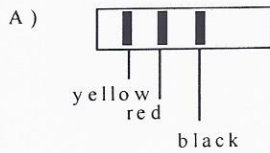2. Which of the resistors illustrated below has a resistance of 4200Ω ?



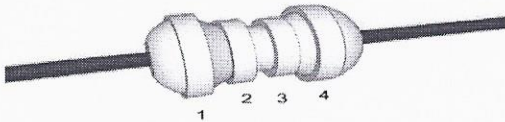3. A diagram of a coded resistor, with each coloured band labelled as a number, is shown below. Resistor




The resistance of this resistor is $340 \Omega \pm 5\%$. What is the colour of the third band on the resistor?

- A) Black **B) Brown** C) Orange D) Red


4. Calculate the equivalent resistance that could replace three resistors in each of the circuits.

Circuit 1

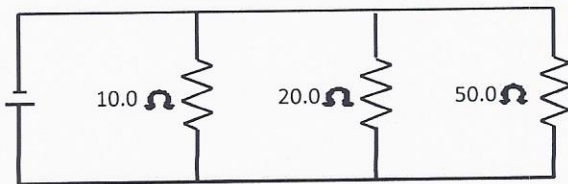


$$\frac{1}{50} + \frac{1}{20} + \frac{1}{10} = 5.88 \Omega$$

Circuit 2

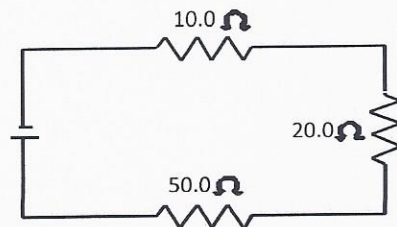

$$50 + 20 + 10 = 80 \Omega$$

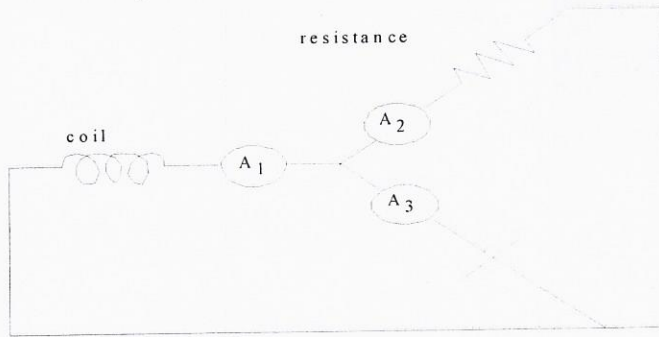
5. Two electrical appliances and a power source are set up as shown on the diagram below.
 Three ammeters are installed in the circuit.
 Ammeter A_1 shows value I_1 .
 Ammeter A_2 shows value I_2 .
 Ammeter A_3 shows value I_3 .



What relation exists among the three values?

- A) $I_3 = I_1 + I_2$ B) $I_1 = I_2 - I_3$ C) $I_2 = I_1 + I_3$ D) $I_1 = I_2 + I_3$

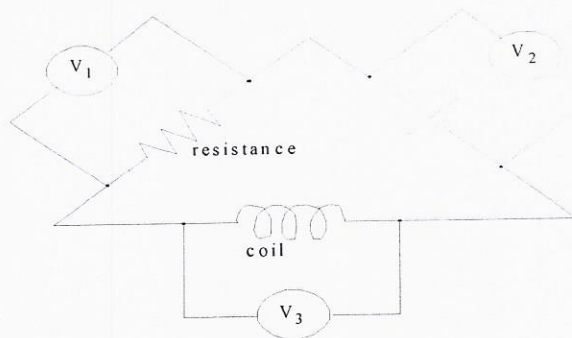
6. Two electrical appliances and a power source are set up as shown on the diagram below.
 Three voltmeters are installed in the circuit.
 Voltmeter V_1 shows value V_1 .
 Voltmeter V_2 shows value V_2 .
 Voltmeter V_3 shows value V_3 .



What relation exists among the three values?

- A) $V_1 = V_2 + V_3$ B) $V_2 = V_1 + V_3$ C) $V_3 = V_1 + V_2$ D) $V_1 = V_2 + V_3$

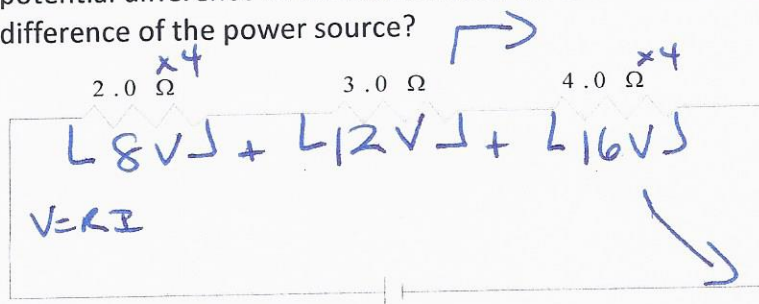7. Three known resistances are connected in series to the terminals of a power source. The potential difference at the terminals of the 3.0Ω resistance is 12 V . What is the potential difference of the power source?



$$I = \frac{V}{R} = \frac{12}{3.0} = 4 \text{ A}$$

$$V_t = R_{tot} \times I_t$$


$$9 \times 4 = 36 \text{ V}$$

$$V_t = V_1 + V_2 + V_3$$

$$8 + 12 + 16 = 36 \text{ V}$$

$$R_{tot} = (4+3+2) = 9 \Omega$$

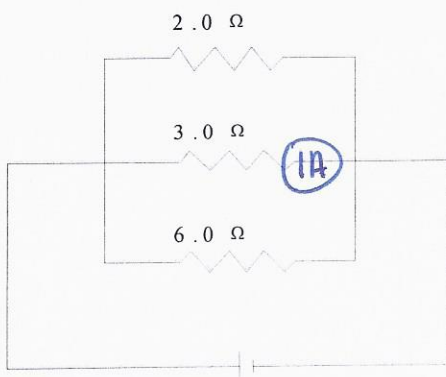8. Three known resistances are connected in parallel to the terminals of a power source. The current passing through the $3.0\ \Omega$ resistance is $1.0\ \text{A}$.




$$V = RI \quad 3 \times 1 = 3V$$

$$I_T = \frac{V_T}{R_T} \quad \frac{3}{1} = 3A$$

$$\frac{1}{2} + \frac{1}{3} + \frac{1}{6} = 1\Omega$$

What is the intensity of the current coming from the power source?

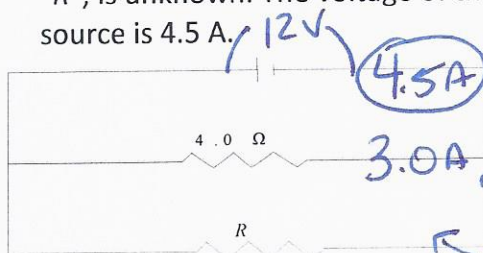9. In the following electric circuit, one of the two resistances is $4.0\ \Omega$. The other resistance, "R", is unknown. The voltage of the power source is $12\ \text{V}$ and the electric current from the source is $4.5\ \text{A}$.




$$R = \frac{V}{I} \quad \frac{12}{1.5} = 8\Omega$$

$$I = \frac{V}{R} \quad \frac{12}{4} = 3.0A \quad 4.5 - 3 = 1.5A$$

What is the value of resistance "R"?

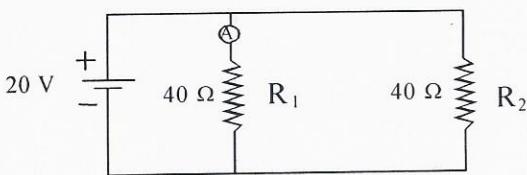
10. The electric circuit shown below consists of an ammeter A, a power supply, and resistors R_1 and R_2 connected in parallel.



$$I = \frac{V}{R} \quad \frac{20}{40} = 0.5A$$

What is the current intensity (I) flowing through the ammeter?

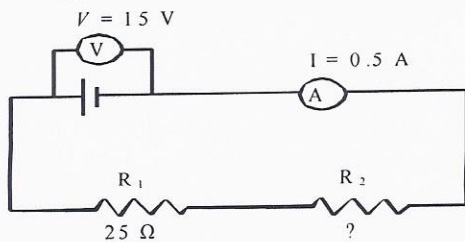11. The following circuit consists of a battery, two resistors (R_1 and R_2), a voltmeter V and an ammeter A . The voltmeter reads $15\ \text{V}$ and the ammeter reads $0.5\ \text{A}$.




$$R_T = \frac{V_T}{I_T} \quad \frac{15}{0.5} = 30\Omega$$

$$30 - 25\Omega = 5\Omega$$


What is the resistance of resistor R_2 ?

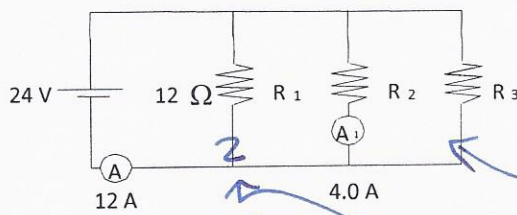12. A circuit consisting of 3 resistors R_1 , R_2 and R_3 , connected in parallel is illustrated below. The power supply is fixed at 24 V. According to this diagram, what is the value of the resistance of resistor R_3 ?



$$R = \frac{V}{I} = \frac{24}{6} = 4\Omega$$

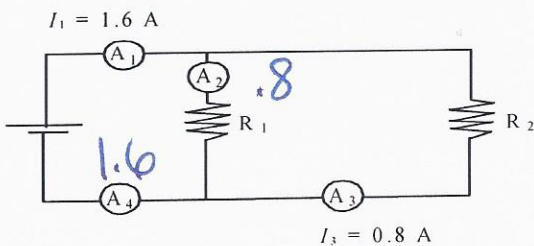
13. The following electric circuit consists of a power source, two identical resistors (R_1 and R_2) and four ammeters A_1 , A_2 , A_3 and A_4 .



Ammeter A_1 reads 1.6 A and ammeter A_3 reads 0.8 A. What do ammeter A_2 and ammeter A_4 read?

- A) Ammeter A_2 reads 0.8 A and ammeter A_4 reads 0.8 A.
- B) Ammeter A_2 reads 0.8 A and ammeter A_4 reads 1.6 A.
- C) Ammeter A_2 reads 1.6 A and ammeter A_4 reads 1.6 A.
- D) Ammeter A_2 reads 1.6 A and ammeter A_4 reads 2.4 A.

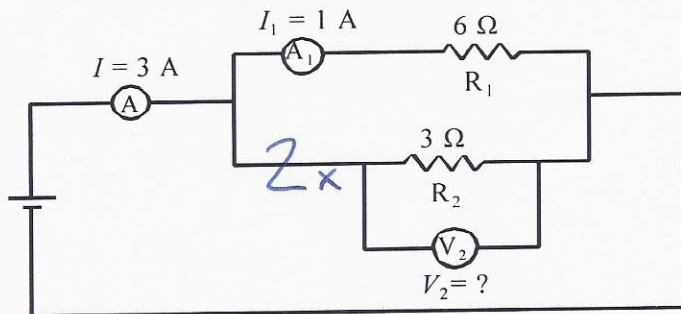14. The following electric circuit consists of a power source, two ammeters (A and A_1), two resistors (R_1 and R_2) and a voltmeter (V_2). Ammeter A reads 3 A and ammeter A_1 reads 1 A. What is the potential difference (voltage), V_2 , across the terminals of resistor R_2 ?




$$V = RI$$


$$6 \times 1 = 6V$$

15. The following two electric circuits consists of a power supply, V_T , an ammeter (A_1) and two identical resistors (R_1 and R_2).

Circuit 1

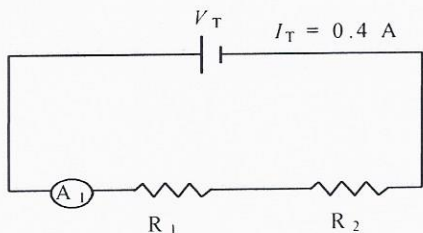



Circuit 2

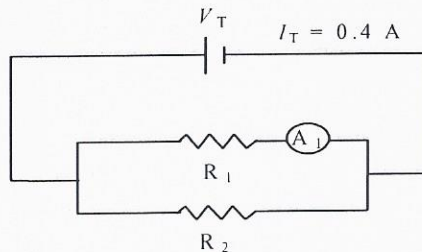

The total current intensity, I_T , in both circuits is 0.4 A.



What is the current intensity reading given by ammeter (A_1) in each circuit?

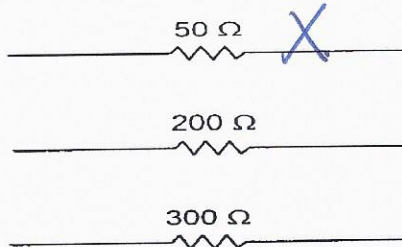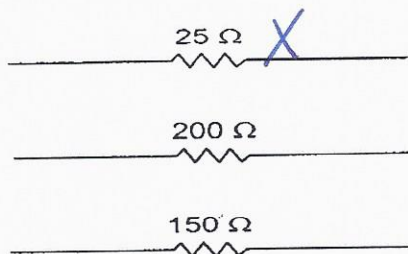- A) The ammeter reads 0.2 A in Circuit 1 and 0.2 A in Circuit 2.
 B) The ammeter reads 0.2 A in Circuit 1 and 0.4 A in Circuit 2.
 C) The ammeter reads 0.4 A in Circuit 1 and 0.2 A in Circuit 2.
 D) The ammeter reads 0.4 A in Circuit 1 and 0.4 A in Circuit 2.
16. In the laboratory, you are given a power supply ($\text{---} \text{---}$), conducting wires and the six resistors shown below.



Using the power supply and two of these resistors, you must build **two** circuits that each have an equivalent resistance of 100 Ω .
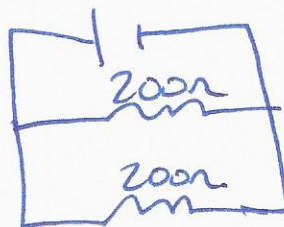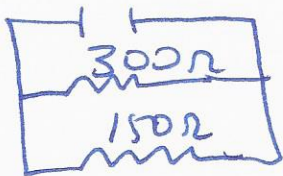
$$\frac{1}{300} + \frac{1}{150} = 100 \Omega$$





$$\frac{1}{200} + \frac{1}{200} = 100 \Omega$$

17. As the values of manufactured resistors are never perfectly precise, they are manufactured with a certain tolerance.

Determine, in order from left to right, the band colors of a resistor if it had a true resistance value of $520 \Omega \pm 5\%$.


Green - red - brown - gold

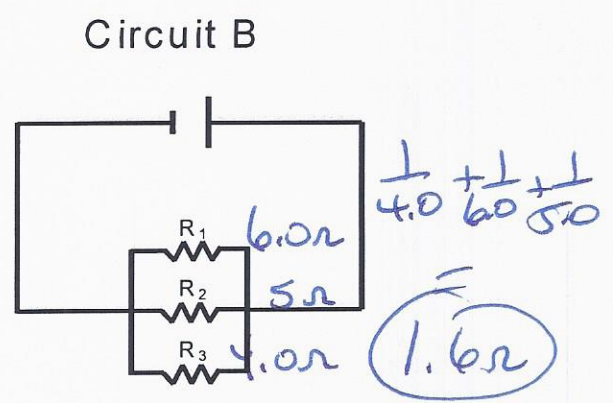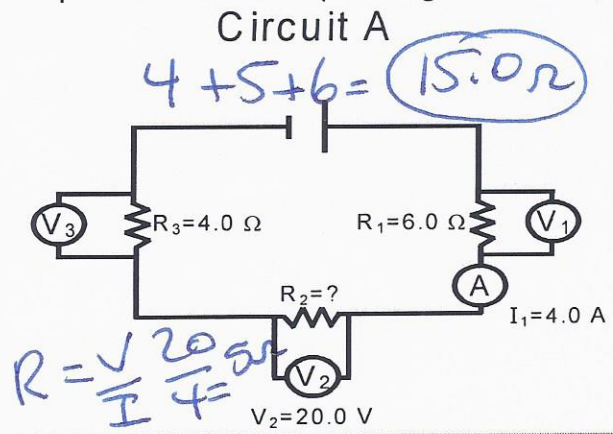18. A student is asked to create two circuits using the same three resistors. He sets up Circuit A so that all the resistors are in series. He then takes it apart and places these same resistors in parallel in Circuit B. (See diagrams below.)




Calculate the equivalent resistance (R_{eq}) of Circuit A and Circuit B.

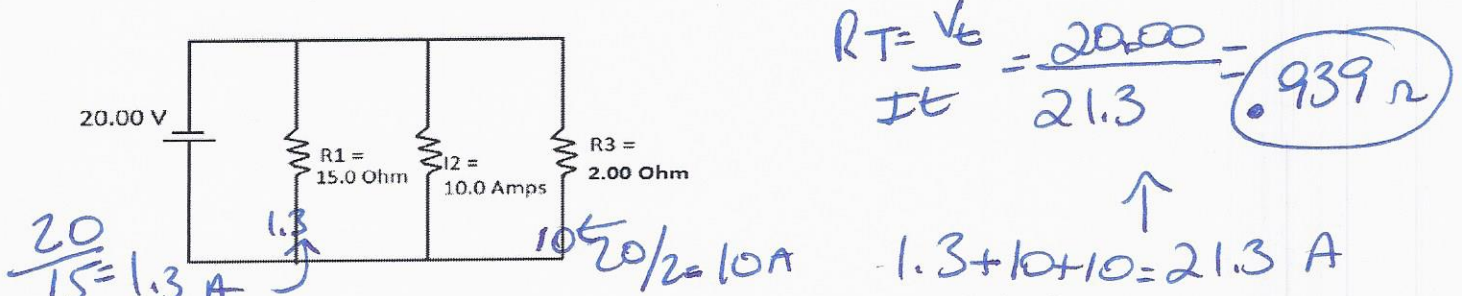19. Calculate the equivalent resistance of the circuit below.




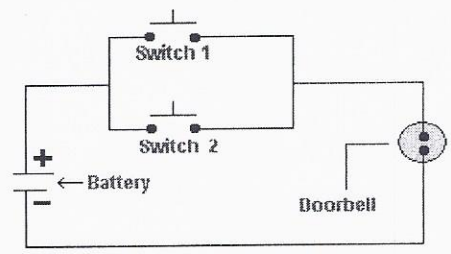20. Which switch must be closed for the doorbell to ring in the circuit below?



Either switch 1 or switch 2.

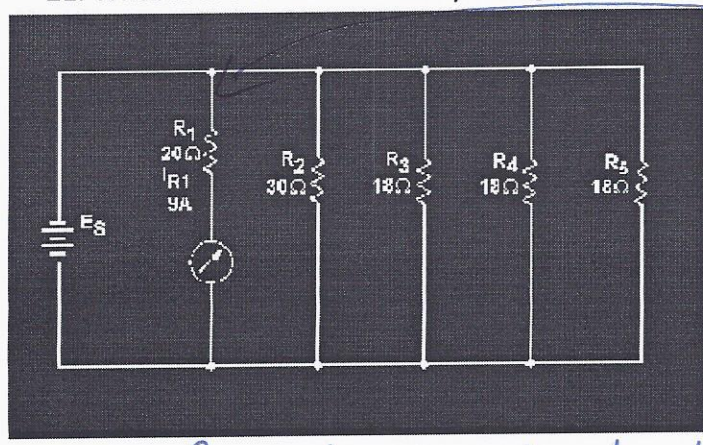21. What is the current intensity for R_3 and the current intensity from the power source?



Handwritten calculations for question 21:
 $V = RI$
 $20 \times 9 = 180 \text{ V}$
 $I_T = \frac{V_T}{R_T} = \frac{180}{4} = 45 \text{ A}$
 $I_3 = \frac{V}{R} = \frac{180}{18} = 10 \text{ A}$

Handwritten calculation for equivalent resistance in question 21:
 $R_T = \frac{1}{\frac{1}{20} + \frac{1}{30} + \frac{1}{18} + \frac{1}{18} + \frac{1}{18}} = 4 \Omega$